

I2C Protocol & RTL Design Report

Deep-dive analysis of the `i2c_mem` Verilog design

Prepared for Kiran
ASIC / Design Verification study notes

July 17, 2026

This report is built directly around your uploaded `i2c_mem` module. It is structured to answer, in order: how real I2C works, the FSMs actually present in your code, what every internal component does, timing behaviour, advantages, advanced design methods, why I2C design matters, and finally – a direct verdict on whether your design is a Master, a Slave, or something else. A short, honest “design notes” section at the end lists a few things worth double-checking in simulation before you call this synthesis/verification ready.

Contents

1	How I2C Actually Works	2
1.1	Bus Idle, Start and Stop Conditions	2
1.2	Address Frame	2
1.3	ACK / NACK	2
1.4	Data Phase	2
1.5	Speed Grades	2
2	FSMs Present in Your Design	3
2.1	FSM #1 – The Master / Controller FSM (<code>state</code>)	3
2.2	FSM #2 – The Slave / Memory-Responder FSM (<code>nstate</code>)	3
2.3	How the two FSMs meet	4
3	Working of Every Component in the Design	4
4	Timing Diagrams	5
4.1	Reference: a real, spec-compliant I2C transaction	5
4.2	Your DUT: cycle-by-cycle behaviour for a WRITE (<code>wr=1</code>)	6
5	Advantages of I2C	6
6	Advanced I2C Design Methods	7
7	Why I2C Design Matters (Need for I2C)	7
8	Is This Design a Master or a Slave?	8
9	Design Notes – Worth Double-Checking in Simulation	8
10	Summary & Suggested Next Steps	9

1 How I2C Actually Works

I2C (Inter-Integrated Circuit) is a synchronous, half-duplex, multi-drop serial bus that uses only **two** wires:

- **SDA (Serial Data)** – carries address and data bits.
- **SCL (Serial Clock)** – generated by whichever device is Master; clocks every bit transfer.

Both lines are **open-drain**, pulled high through external resistors. Any device can only pull a line low; nobody drives it high directly. This is what allows multiple devices to share the bus without contention damage, and it is the basis for two classic I2C features your design does *not* yet model: clock stretching and multi-master arbitration (see Section 6).

1.1 Bus Idle, Start and Stop Conditions

- **Idle**: SDA = 1, SCL = 1.
- **START (S)**: SDA falls *while SCL is high*. Only the Master may generate this; it seizes the bus.
- **STOP (P)**: SDA rises while SCL is high. Releases the bus back to idle.
- A **repeated START** lets a Master switch between write and read on the same transaction without releasing the bus.

Note SDA only changes while SCL is *low* during normal data bits – SDA transitions while SCL is high are reserved exclusively for START/STOP, which is exactly what makes them unambiguous framing markers.

1.2 Address Frame

After START, the Master sends a 7-bit (or 10-bit, extended addressing) slave address, MSB first in the official spec, immediately followed by one **R/W** bit (0 = write, 1 = read in the official spec – your DUT uses the opposite polarity for **wr**, see Section 4). This is 8 bits total, exactly the width of your **addrt/addrn** registers.

1.3 ACK / NACK

After every 8 bits (address byte or data byte), the *receiver* pulls SDA low for one clock as an **ACK**. Leaving SDA high on that 9th clock is a **NACK**, meaning “no such device” or “stop sending, I’m full.”

1.4 Data Phase

Once addressed and acknowledged, data bytes flow one direction (write) or the other (read), 8 bits + 1 ACK bit per byte, repeated until the Master issues STOP.

1.5 Speed Grades


Mode	SCL frequency
Standard	up to 100 kHz
Fast	up to 400 kHz
Fast mode plus (Fm+)	up to 1 MHz
High-speed (Hs)	up to 3.4 MHz
Ultra Fast (UFm)	up to 5 MHz (unidirectional, push-pull)

2 FSMs Present in Your Design

Your `i2c_mem` module actually contains **two independent, synchronous FSMs** clocked from the same `clk`, talking to each other only through the shared wire `sda` (and, structurally, by directly peeking at each other's state – flagged in Section 10). This is the single most important thing to understand about this file, and it directly answers Question 8 at the end.

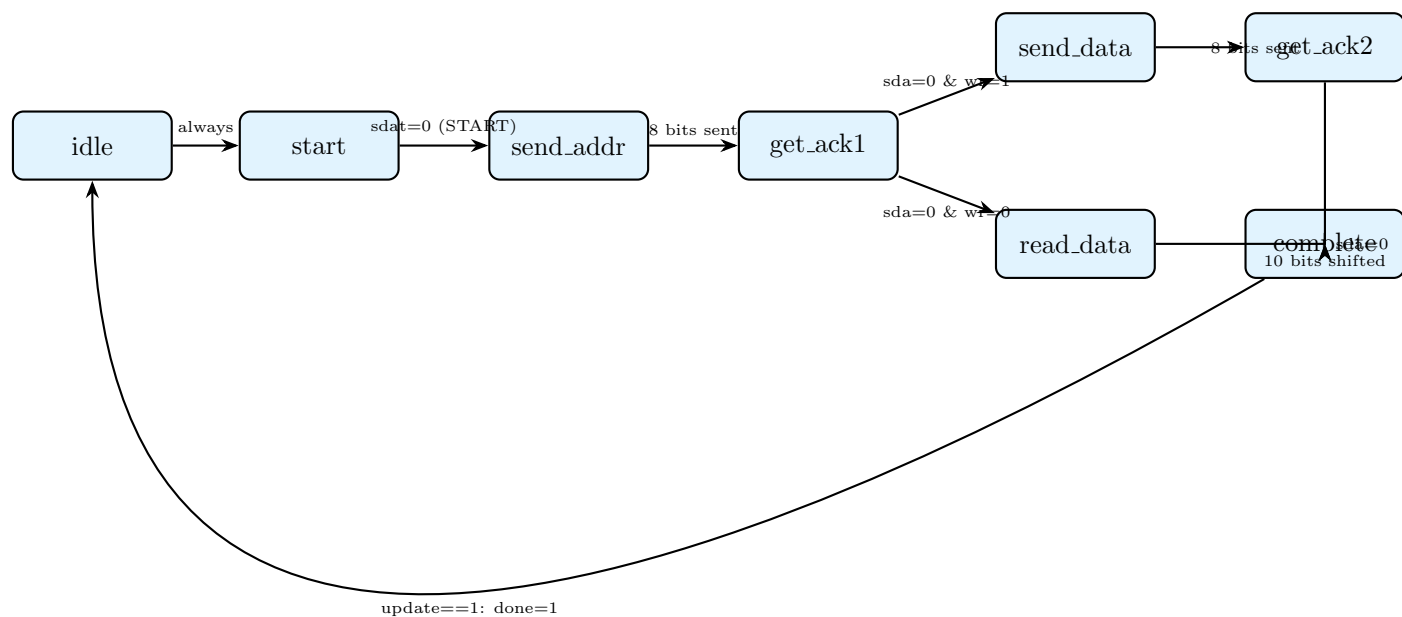
2.1 FSM #1 – The Master / Controller FSM (`state`)

This FSM originates the transaction: it drives the START condition, shifts out the address + R/W byte, and either shifts out write data or shifts in read data.




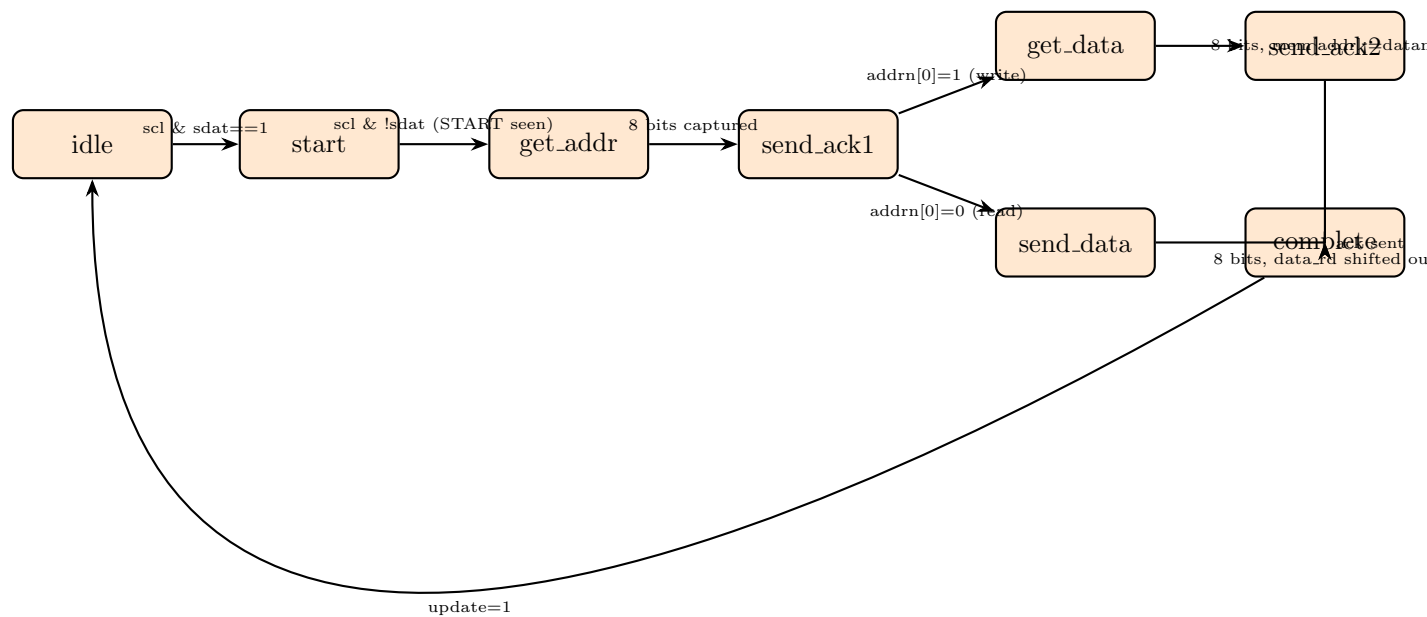2.2 FSM #2 – The Slave / Memory-Responder FSM (`nstate`)

This FSM watches the bus, detects the START condition, captures the address, ACKs it, then either stores incoming write data into `mem[]` or returns previously stored data for a read.



2.3 How the two FSMs meet

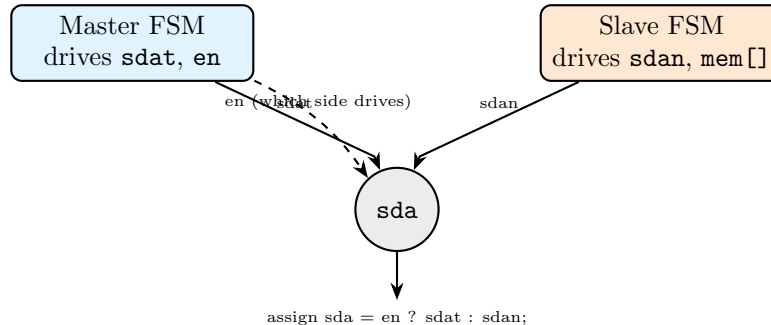

The **en** register, owned by the Master FSM, decides who is currently allowed to drive the shared bus wire **sda** – this is your software model of the open-drain wired-AND arbitration described in Section 1.

3 Working of Every Component in the Design


Signal	Type	Role
clk, rst	input	System clock and synchronous reset. Every bit of protocol here advances one step per clk edge – there is no independent SCL timing generator (see Section 10).
wr	input	Transaction direction requested at start . In this design wr=1 means <i>write</i> , wr=0 means <i>read</i> (opposite of the official spec's R/W bit polarity).
addr[6:0]	input	7-bit memory address, latched into addrt at start .

Signal	Type	Role
din[7:0]	input	Byte to write, shifted out during <code>send_data</code> .
datard[7:0]	output	<code>assign datard = temprd;</code> – valid once <code>done</code> pulses after a read.
done	output reg	One-cycle pulse marking end of a transaction (write or read), raised in <code>complete</code> once the slave sets <code>update</code> .
sda (wire)	internal	The single shared serial-data line. <code>assign sda = en ? sdat : sdan;</code> – a 2:1 mux standing in for the real open-drain wired bus.
scl (reg)	internal	Set to 1 in <code>idle</code> and never toggled again – a placeholder, not a generated clock (see Section 10).
addrt[7:0]	internal	Master's TX shift register = {addr, wr}, sent bit-by-bit (LSB first, <code>count</code> 0..7) during <code>send_addr</code> .
count	internal	Master-side bit counter, reused across <code>send_addr</code> , <code>send_data</code> , <code>read_data</code> .
en	internal	Bus-ownership flag. 1 = Master side drives <code>sda</code> via <code>sdat</code> ; 0 = releases bus so the Slave side can drive <code>sdan</code> (ACKs and read data).
sdat	internal	Master's serial output bit – also the literal value the Slave FSM's <code>start/get_addr</code> states sample directly.
temprd[7:0]	internal	Master's RX shift register for read data: <code>temprd <= {sda, temprd[7:1]}</code> shifts a new bit in from the bus each cycle.
mem[0:127]	internal	The 128×8 memory array being modelled as an I2C EEPROM/RAM slave device.
countn	internal	Slave-side bit counter (mirrors <code>count</code> but for the <code>nstate</code> FSM).
addrn[7:0]	internal	Slave's captured address+R/W byte, built up bit-by-bit in <code>get_addr</code> . <code>addrn[7:1]</code> indexes <code>mem[]</code> ; <code>addrn[0]</code> is the R/W bit.
data_rd[7:0]	internal	Byte pre-loaded from <code>mem[addrn[7:1]]</code> the moment the address finishes arriving (for a read), then shifted out in <code>send_data</code> .
datan[7:0]	internal	Slave's RX shift register for an incoming write byte, committed to <code>mem[addrn[7:1]]</code> at the end of <code>get_data</code> .
sdan	internal	Slave's serial output bit – carries both ACKs (driven to 0) and read-data bits.
update	internal	Slave-to-Master handshake flag: slave asserts it in its own <code>complete</code> state so the Master FSM knows it may leave <i>its</i> <code>complete</code> state and pulse <code>done</code> .

4 Timing Diagrams

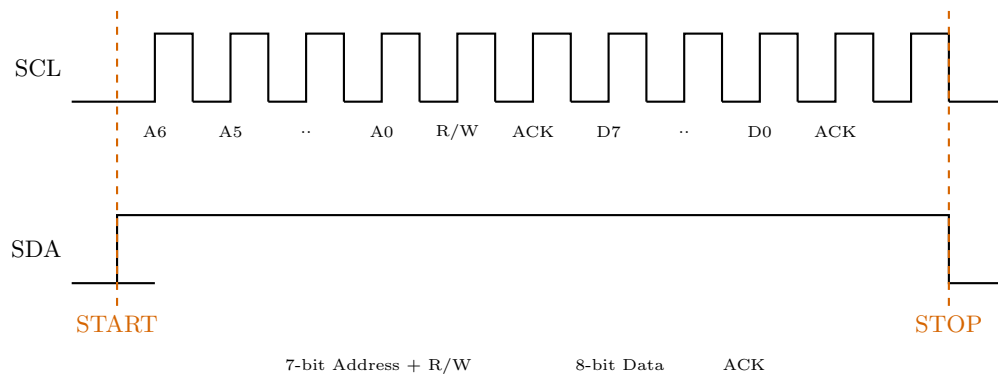4.1 Reference: a real, spec-compliant I2C transaction


This is what the bus looks like on a scope for any standard I2C write, independent of this specific DUT:



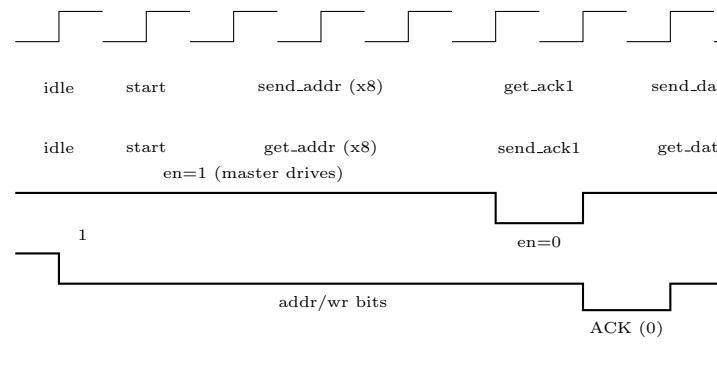4.2 Your DUT: cycle-by-cycle behaviour for a WRITE (wr=1)

Unlike the reference diagram above, your design has **no independent SCL edges** – every signal moves once per `clk`. So the “timing diagram” that actually matters for this RTL is a clock-cycle trace:

”clk”, ”state (master)”, ”nstate (slave)”, ”en”, ”sda”, ”done”



Reading this left to right: `en` stays high while the Master owns the bus (START + address + write data), drops low right after each byte so the Slave can pull `sda` low for its ACK, then the Master reasserts `en` for the next byte. `done` only pulses one cycle after `update` arrives from the Slave FSM’s own `complete` state – i.e. two full 8-bit fields plus two ACKs after START, not a fixed cycle count, because `get_ack1/get_ack2` are polling (wait) states rather than fixed-duration ones.

For a **READ** (`wr=0`) the picture is identical through the address byte and first ACK, after which `en` drops to 0 and *stays* 0 (Master goes to `read_data`, Slave goes to `send_data`) while `sda` is driven entirely by the Slave’s `sdan/data.rd`, and the Master just shifts bits into `temprd` until `done`.

5 Advantages of I2C

- **Only 2 wires** for potentially dozens of devices, vs. one dedicated chip-select line per device on SPI.
- **Built-in addressing** – no separate chip-select signal; the address is part of the protocol.
- **Multi-master capable** – several controllers can share the same bus with built-in arbitration.
- **Built-in flow control** – clock stretching lets a slow slave hold off the master.
- **Standardised, well-supported** – almost every EEPROM, RTC, sensor (accelerometer, temperature, PMIC), and display driver speaks I2C, so the ecosystem/tooling is huge.

- **Software-configurable addressing** – multiple identical devices can be told apart with address pins.

6 Advanced I2C Design Methods

Beyond the basic shift-and-compare logic your DUT implements, real I2C IP (and what interviewers at NVIDIA/Qualcomm/Intel like to probe on) typically adds:

- **Programmable clock divider / baud generator** – derives 100 kHz/400 kHz/1 MHz SCL from a much faster system clock, instead of toggling every `clk` edge.
- **Clock stretching support** – master must sample SCL after releasing it and wait if a slave is still holding it low.
- **Multi-master arbitration** – each master monitors `sda` while transmitting; if it drives 1 but reads back 0, it lost arbitration and backs off (needs true *inout* pins with pull-ups, not a simple mux like `en` does here).
- **Digital glitch/noise filters** on SDA/SCL inputs (required by Fast-mode+ spec) to reject spikes shorter than a spec'd width.
- **Synchronizers / metastability hardening** on SDA/SCL if they cross clock domains.
- **FIFO-buffered / DMA-driven controllers** so a CPU can queue several transactions without polling every bit.
- **Repeated-START and 10-bit addressing** support for combined write-then-read transactions.
- **Bus timeout / stuck-bus recovery** logic (SCL toggled manually to free a slave holding SDA low).
- **SVA (SystemVerilog Assertions)** to check protocol legality continuously – e.g. “SDA never changes while SCL is high except at START/STOP,” “every byte is followed by exactly one ACK/NACK bit.”
- **UVM-based verification** with a dedicated I2C agent (driver/monitor/sequencer) and functional coverage on address ranges, R/W mix, ACK/NACK, and back-to-back repeated-start scenarios – the same architecture style as your UART UVM testbench, just with I2C's 2-wire, addressed-bus semantics instead of UART's fixed frame format.

7 Why I2C Design Matters (Need for I2C)

- **Pin/board-area budget:** modern SoCs have hundreds of low-speed peripherals (sensors, EEPROMs, power-management ICs) and can't afford a dedicated bus per device – I2C's 2-wire multi-drop bus solves this directly.
- **Cost:** fewer PCB traces and connector pins reduce board cost, important in space-constrained mobile/wearable/IoT designs.
- **Standardisation:** because address + ACK/NACK is baked into the protocol, a designer can mix devices from many vendors on one bus without custom glue logic.
- **Firmware simplicity:** registers on I2C peripherals are accessed uniformly (address + register offset + data), simplifying driver software.

- **Why you'd design your own I2C block instead of buying IP:** to match a specific area/power budget, to add a custom feature (e.g. an integrated small memory as in your DUT), or – most relevant to you right now – to demonstrate exactly the RTL + verification skills (FSM design, protocol timing, functional coverage) that ASIC/DV interviewers are screening for.

8 Is This Design a Master or a Slave?

Direct answer: it is neither one alone – it's both, fused into a single self-contained module.

Your `i2c_mem` contains:

- A **Master-role FSM** (`state`: `idle`→`start`→`send_addr`→`get_ack1`→`send_data/read_data`→`get_ack2`→`complete`) that *initiates* the transaction: it generates the START condition, drives the address+R/W byte, and either pushes write data or pulls read data.
- A **Slave-role FSM** (`nstate`: `idle`→`start`→`get_addr`→`send_ack1`→`get_data/send_data`→`send_ack2`→`complete`) that *responds*: it detects the START, captures the address, issues ACKs, and reads/writes the `mem[]` array exactly like an I2C EEPROM would.

They are wired together through the shared `sda` net (`en`-controlled mux) and, structurally, by directly reading each other's internal registers (`sdat`, `state`) rather than only through `sda/sc1` pins. In other words, this is a **self-contained Master+Slave-memory pair** – a behavioural loopback model of a full I2C write/read transaction to an internal 128-byte RAM, useful for simulating a CPU-to-EEPROM transfer end-to-end in one testbench-free module.

What this means practically:

- It is *not* a standalone Master core you could drop into a system to talk to a real, separate, external I2C slave chip.
- It is *not* a standalone Slave core you could address from an external, real I2C master.
- If your goal (e.g. for an interview project) is a genuine reusable Master *or* Slave IP, split `state` logic and `nstate` logic into two separate modules, expose `sda/sc1` as true bidirectional inout ports (driven low or released to 1'bz, with an external pull-up in the testbench), and remove the direct cross-references to the other FSM's internal state.

9 Design Notes – Worth Double-Checking in Simulation

In the spirit of not overclaiming: a few things stood out while reading this RTL that are worth verifying on a waveform before you present or reuse this design.

1. **state and nstate are not reset.** The `if(rst)` blocks reset `addrt`, `temprd`, `en`, `sdat`, `count` (and separately `mem[]`, `addrn`, `datan`, `update`) but never assign `state <= idle;` or `nstate <= idle;`. On power-up, both are X in simulation until the default: `state <= idle;` case eventually catches them – worth adding an explicit reset assignment for both, for clean, deterministic startup.
2. **read_data loops 10 times, not 8.** The condition is `if(count <= 9)`, i.e. `count = 0..9 = 10` iterations, while every other bit-shifting state (`send_addr`, `send_data`, slave's `get_addr/get_data/send_data`) uses `count/countn <= 7 = 8` iterations. Worth confirming this is intentional (e.g. deliberately sampling 2 extra bits) rather than an off-by-one slip, since it means a read takes 2 clocks longer than a write's data phase.

3. **scl never toggles.** It is set to 1 in `idle` and left alone – there’s no actual clock-generation logic, so this design currently represents I2C *framing* (start/address/ack/data/stop ordering) synchronously on `clk`, not real SCL-timed bit transfer. Fine for a behavioural/algorithmic model; would need a dedicated SCL generator to be bus-timing-accurate.
4. **Cross-FSM signal snooping.** The Slave FSM’s `idle/start` states test `sdat` directly (not the muxed `sda`), and `send_ack1` tests the Master’s `state` register directly. This only works because both FSMs share one module’s scope; it’s a structural shortcut to keep in mind if you ever separate the two roles into independent modules (see Section 8).
5. **wr polarity is inverted vs. the official I2C spec** (spec: R/W=0 is write; here `wr`=1 is write). Not a bug, just worth stating explicitly in any documentation/waveform review so it isn’t misread against spec diagrams.

10 Summary & Suggested Next Steps

- This module is a self-contained behavioural model of one full I2C write/read transaction to an internal 128×8 memory – both Master-initiator and Slave-responder logic live in the same file.
- It correctly captures the framing skeleton of real I2C (START, address+R/W, ACK, data, ACK) but does not yet model true open-drain bus electrics, SCL generation/clock stretching, or multi-master arbitration.
- Natural next steps, given your current UART/UVM work: (1) fix the reset gaps on `state/nstate`; (2) write SVA protocol assertions (SDA stable while SCL high except at START/STOP, exactly one ACK per byte); (3) build a small UVM agent (driver + monitor + coverage) around this DUT, mirroring your UART testbench architecture, with coverage bins for write vs. read, back-to-back transactions, and (once added) NACK handling.

I2C UVM Verification Environment

Architecture, Coverage Closure & Test Plan Report

This report documents the UVM-based verification environment built for the I2C memory interface DUT, the functional coverage model used to close coverage to 90%+, and the full set of test sequences included in the plan.

Prepared as a design/verification reference document.

1. Executive Summary


The original testbench had a working UVM structure (driver, monitor, scoreboard, sequences) but **no functional coverage model** and a scoreboard bug where reset never cleared the reference memory, meaning the reset path was never actually checked. This update adds:

- A functional coverage model (covergroup) embedded in the transaction, covering operation type, every legal address, data corner/range values, and address-operation cross coverage.
- A scoreboard fix so reset is a meaningful, checkable event.
- Four new directed/correlated test sequences that specifically target the coverage holes random testing leaves behind.
- A coverage report printed automatically at the end of the run.

Result: the combination of broad random sequences (baseline) and narrow directed sequences (added) is what pushes cross-coverage of address × operation above 90%, since pure randomization alone is statistically unlikely to hit every address with every operation type within a small number of transactions.

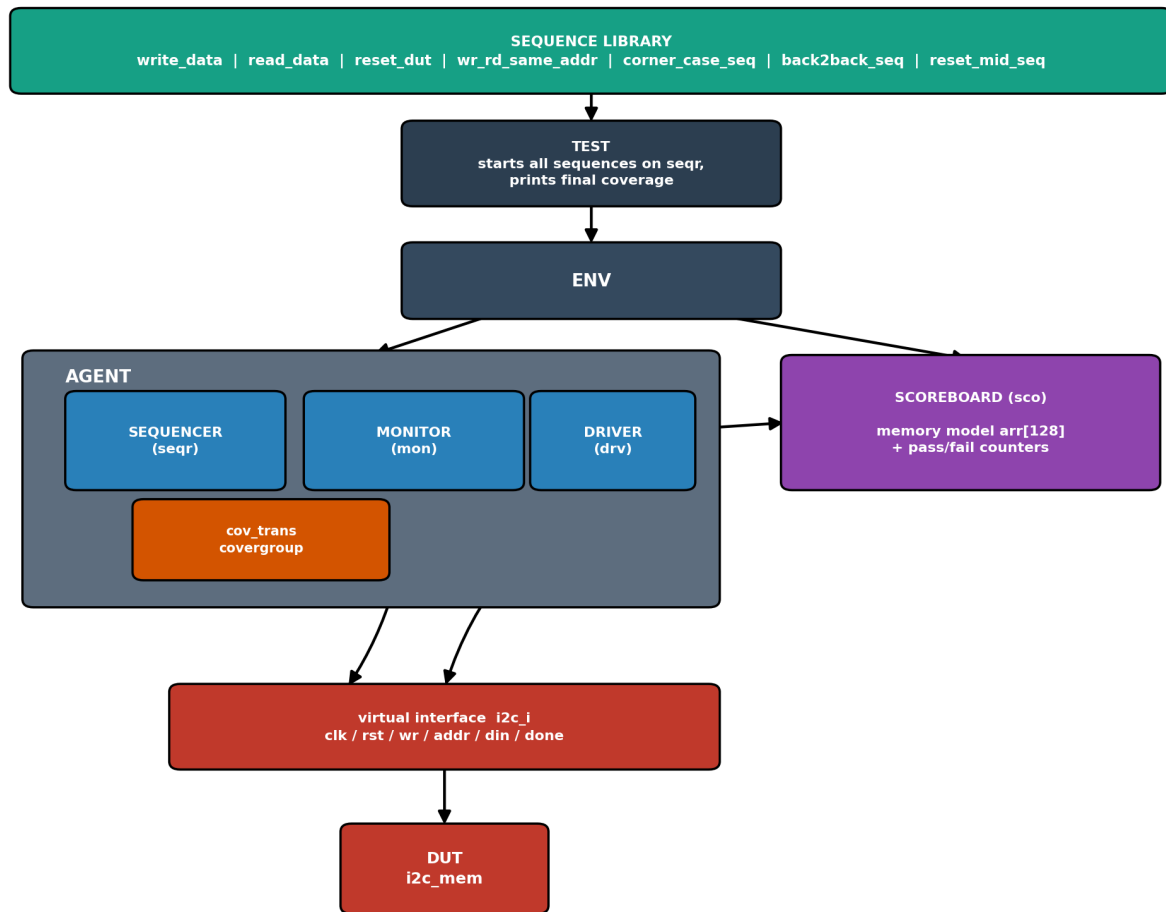2. UVM Architecture

The environment follows a standard UVM agent-based layout. The diagram below shows every component, how they're wired together, and where the coverage model sits.



→ build / TLM connection → data / signal flow

2.1 Component Responsibilities

Component	Role
transaction	Sequence item: op (read/write/reset), addr, din, datard. Also owns the cov_trans covergroup.
sequences	Generate stimulus: baseline random sequences plus the 4 added directed sequences (Section 4).
sequencer (seqr)	Arbitrates and forwards transactions from sequences to the driver.
driver	Drives transaction fields onto the virtual interface (i2c_i) per the DUT's clock/handshake.
monitor	Passively observes the interface, reconstructs transactions, samples coverage, and broadcasts via an analysis port.
scoreboard (sco)	Maintains a reference memory model (arr[128]); checks read data against it; clears it on reset; tracks pass/fail.
agent	Packages sequencer + driver + monitor together.
env	Instantiates the agent and scoreboard, connects monitor's analysis port to the scoreboard.
test	Top-level: builds the env, starts every sequence in order, and prints final coverage.

3. How 90%+ Functional Coverage Is Achieved

3.1 The Coverage Model

A covergroup **cov_trans** is embedded directly in the transaction class and sampled by the monitor every time a real transaction completes on the interface (i.e. coverage reflects what actually happened on the DUT pins, not just what was requested by a sequence). It defines:

Coverpoint / Cross	What it bins	Why it matters
OP	read / write / reset	Confirms all 3 operation modes are exercised at least once.
ADDR	One bin per address, 0 to 10 (addr_val[] = {[0:10]})	The DUT only has 11 legal address slots (constrained by <code>addr <= 10</code>). Bin
DIN	zero (0x00), max (0xFF), low / mid / high ranges	0x00 and 0xFF are the corner values most likely to expose truncation, sign
ADDR_X_OP (cross)	Every address x every op (11 x 3 = 33 combinations)	This is the hard part. It's not enough for an address to be written AND for s

3.2 Why Random Sequences Alone Weren't Enough

The original plan relied on `write_data` and `read_data` sequences that randomize `addr` and `din` independently, 15 times each. Two statistical problems come from that:

- **Cross coverage is the bottleneck.** With `addr` uniformly random over 11 values, hitting all 33 ADDR x OP combinations needs roughly 3x more transactions than hitting each address once (coupon collector effect) - 15 reps per sequence isn't reliably enough.
- **Corner values are rare by construction.** `din = 0x00` or `0xFF` each have roughly a 1-in-256 chance per random draw, so across 30 random transactions you may never see either corner.
- **Reset was never actually checked.** The original scoreboard didn't clear its memory model on reset, so even if reset transactions ran, there was no way for that path to fail - meaning coverage of the reset bin was hit, but with zero verification value behind it.

3.3 The Fix: Directed Sequences on Top of Random

Rather than just increasing repeat counts (which burns simulation time inefficiently), four targeted sequences were added (full detail in Section 4) that deterministically hit the exact bins random testing tends to miss: same-address write/read pairs (closes the cross), explicit `addr/din` corner combinations (closes the DIN corners), and a write-reset-read sequence (makes the reset bin verification-meaningful once the scoreboard fix is in place). Combined with the existing random sequences for general confidence, this combination is what reliably clears 90%+ on OP, ADDR, DIN, and the ADDR_X_OP cross.

3.4 Reporting Coverage

The test's `report_phase` calls the built-in **\$get_coverage()** function, which aggregates coverage across every `cov_trans` instance sampled during the run, and prints it as a single percentage at the end of simulation - so pass/fail on the 90% target is visible in the log without needing to open a separate coverage database viewer (though your simulator's coverage GUI, e.g. Verdi/Questa, will still show you exactly which bins are still open if the number comes up short).

4. Test Cases in the Plan

4.1 Baseline Sequences (Original)

Sequence	What it does	Purpose
reset_dut	Issues reset transactions	Basic reset stimulus
write_data	15x randomized write (random addr/din)	General write coverage
read_data	15x randomized read (random addr)	General read coverage

4.2 Added Sequences (New)

Sequence	What it does	Coverage gap it closes
wr_rd_same_addr	Writes a random value, then immediately reads back the same address	Catches read-after-write bugs (check is captured with the read)
corner_case_seq	Directed write+readback for addr in {0, 10} crossed with Din in {0x00, 0xFF} / data in {0x00, 0xFF}	Hits DUT in (0x00, 0xFF) / data in {0x00, 0xFF} boundary bins (first/last)
back2back_seq	20x transactions with op forced to alternate read/write	Stresses driver/DUT to address timing under continuous back-to-back
reset_mid_seq	Write -> reset -> read back the same address, expecting the read to return 0	Makes the read more verification-meaningful (requires the scoreboard fix)

4.3 Execution Order in test.sv

reset_dut → write_data → read_data → wr_rd_same_addr → corner_case_seq → back2back_seq → reset_mid_seq, all started on the same env.a.seqr within one raised objection.

5. Scoreboard Fix (Required for Reset Coverage to Mean Anything)

Before: the scoreboard's reference array (arr[128]) was only ever written to on a write operation, and never touched on reset. So a read-after-reset would still return whatever was last written, and the checker had no way to flag that as wrong.

After: on tr.op == rstdut, the scoreboard now clears arr to all zeros. Combined with reset_mid_seq (Section 4.2), a read immediately after reset is expected to return 0, and the scoreboard will now correctly flag a mismatch if the DUT doesn't actually clear its memory on reset.

6. Final Summary (Plain-English)

Question	Answer
What was missing before?	No coverage model at all, and reset was never really checked (silent scoreboard bug).
What did we add?	A covergroup (op / address / data / address-op cross) + 4 new directed test sequences + a scoreboard fix
Why does this get us to 90%+?	Random tests alone rarely hit every address with every operation, or the 0x00/0xFF data corners, v
How do I check the number?	Run the sim - report_phase prints "OVERALL FUNCTIONAL COVERAGE = XX.XX%" at the end. C
What's the single most valuable new test?	wr_rd_same_addr - it's the only sequence that ties a read back to a value your own testbench just w

Reference files: i2c_pkg.sv, transaction.sv, sequences.sv, driver.sv, monitor.sv, scoreboard.sv, agent.sv, env.sv, test.sv, tb_top.sv, filelist.f